

Subject Name: Computer Organization and Architecture
Subject Code: 25BCA112T

Max. Marks: 25
Time: 1:30 Hrs.

Instructions

- All Questions are Compulsory.
- Scientific calculators not allowed.

CO #	Cognitive Ability	Course Outcome
CO1	Remember	Recall the basic concepts of number systems & codes, terminology of computer organization, architecture, and system components.
CO3	Apply	Apply knowledge of SOP/POS equations & computer system architecture.
CO4	Analyse	Analyze the performance of different SOP/POS equations and system components.

Q 1.	Attempt any 5 out of 7. (1 mark each) a) What is the base of Octal number system? b) Write the answer for given binary subtraction: $(1111)_2 - (1001)_2 = (\dots\dots\dots)_2$ c) Which logic gate follows the given statement? “If one of i/p is logic-1 then the o/p of the gate is logic-1”. d) Which Counter works very slow? (Synchronous or Asynchronous) e) ROM a volatile or non-volatile memory? f) What is the use of buses in computer systems? g) List any two examples of Secondary memories used in computer system.	(5 Marks)	CO1
Q 2.	Attempt any 2 out of 4. (5 marks each) a) Which are Basic gates, Universal Gates & Derived gates? Also draw the symbol & truth table for Universal gates. b) Draw the logic diagrams for Half Adder & Full Subtractor. c) Where are Boolean rules are used? Write any 4 Boolean rules. d) Explain the General block diagram of Daisy chaining priority interrupt.	(10 Marks)	CO3
Q 3.	Attempt any one Question (A or B). (5 marks each) A) i) Convert the given codes step by step: i) $(1011.11)_2 = (\dots\dots\dots)_{10}$ ii) $(35)_8 = (\dots\dots\dots)_{BCD}$ ii) Solve the given Boolean Equation using K-Map & draw the logic diagram for solved equation. $Y_{(ABC)} = \sum (1,3,4,5,7)$ OR B) i) What is need of Cache Memory? Find the average access time for computer, if Hit ratio is 90%. Given: Cache memory Access time, $T_c = 20\mu s$ & Main memory Access time, $T_m = 100\mu s$ ($\mu s = \text{Microseconds}$). ii) What is need of memory in computer system? Explain with suitable diagram 3-level memory hierarchy.	(10 Marks)	CO4
