

INDIRA UNIVERSITY, PUNE

SCHOOL OF INFORMATION TECHNOLOGY-BSC (CYS)

Term End Examination (2025 Pattern) December – 2025 - Semester – I

Subject Name: Computer Organization & Architecture

Max. Marks: 25

Subject Code: 25CYS109T

Time: 1:30 Hrs.

Instructions

- All Questions are Compulsory.

CO #	Cognitive Ability	Course Outcome
CO1	Remember	Recall the basic concepts of number systems & codes, terminology of computer organization, architecture, and system components.
CO3	Apply	Apply knowledge of SOP/POS equations & computer system architecture.
CO4	Analyse	Analyze the performance of different SOP/POS equations and system components.

Q1.	<p>Attempt any 5 out of 7. (1 mark each) (5 Marks)</p> <p>a) What is a 1's complement of binary number (1010)?</p> <p>b) What is the base of the decimal number system?</p> <p>c) What is the basic difference between Half Adder & Full Adder?</p> <p>d) Define the modulus of the counter.</p> <p>e) Draw the symbol for 2 i/p EX-NOR gates with i/p's A & B?</p> <p>f) List the types of buses used in computer organization.</p> <p>g) Name two types of RAM.</p>	CO1
Q2.	<p>Attempt any 2 out of 4. (5 marks each) (10 Marks)</p> <p>a) Represent the given Gray code (101101) into BCD code and $(A9)_{16}$ to Excess-3 code.</p> <p>b) Determine & mention Boolean laws which are used in simplifying the given Boolean equation & draw the simplified logical diagram. $Y = A' B + A C + B C + B + A' A$ (Here A'= compliment of A)</p> <p>c) Construct & explain the logic circuit diagram of 1:4 De-Mux with active high strobe.</p> <p>d) Construct & explain the general I/O interface diagram.</p>	CO3
Q.3.	<p>Attempt all questions. (5 marks each) (10 Marks)</p> <p>a) Identify the methods used to represent signed binary numbers.</p> <p>b) Analyse the 4-bit ALU block diagram using combinational circuits.</p> <p style="text-align: center;">OR</p> <p>a) Analyse the importance of memory hierarchy in increasing the efficacy of CPU.</p> <p>b) Interpret the Boolean simplification of $Y=(A+B)(A+C)$ and explain the change in gate count.</p>	CO4